

# Digital Design with the Verilog HDL

## Chapter 6 Finite State Machine

Binh Tran-Thanh


Department of Computer Engineering  
Faculty of Computer Science and Engineering  
Ho Chi Minh City University of Technology

May 26, 2023


 
# Sequential Machine - Definition

- State of a sequential machine contains current information ( $t$ )
- Next state ( $t + 1$ ) depends on the current state ( $t$ ) and inputs
- The number of states in a sequential machine finite  $\Rightarrow$  **Finite State Machine - FSM**



Block Diagram of a sequential machine

# Synchronous Sequential Machine

- Synchronous State Machine uses clock to synchronize input states
- Clock is symmetric or asymmetric
- Clock cycle **must be larger than time required for state transaction calculation**
- Synchronous FSMs:
  - Number of states
  - Using clock to control state transaction




# FSM Models & Types

- Explicit
  - Declares a state register that stores the FSM state
  - May not be called “state” –might be a counter!
- Implicit
  - Describes state implicitly by using multiple event controls
- Moore
  - Outputs depend on state only (synchronous)
- Mealy
  - Outputs depend on inputs and state (asynchronous)
  - Outputs can also be registered (synchronous)




# Mealy machine vs. Moore machine
 
## Block Diagram of a Mealy sequential machine


 
## Block Diagram of a Moore sequential machine




# State Transaction Graph

- Finite state machine can be described:
  - State transaction graph, State transaction table
  - Time chart
  - Abstract state machine
- Finite state machine is a directed graph
  - Vertices show states (+outputs if Moore-style machine)
  - Edges show transactions from state to state
- Edges' name
  - Mealy machine: input/output
  - Moore machine: input



 
## State Diagram: Mealy

- Outputs Y and Z are 0, unless specified otherwise.
- We don't care about the value of b in S0, or the value of a in S1, or either a or b in S2.


 
# State Diagram: Moore


- Outputs Y and Z are 0, unless specified otherwise.
- If an input isn't listed for a transition, we don't care about its value for that transition





## Example - Mealy

State transition graph

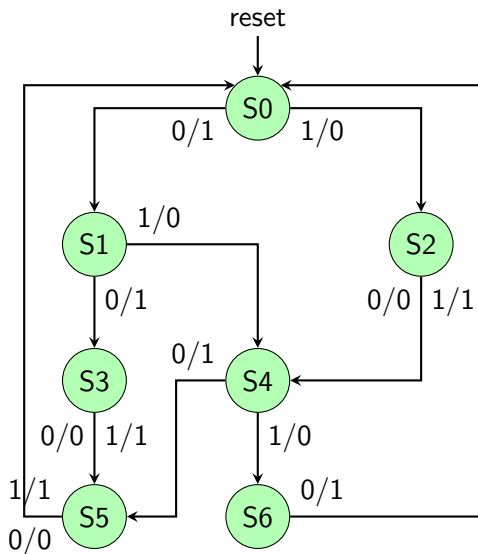


State transition table


State	Next state/ output	
	input	
	0	1
S0	S1/1	S2/0
S1	S3/1	S4/0
S2	S4/0	S4/1
S3	S5/0	S5/1
S4	S5/1	S6/0
S5	S0/0	S0/1
S6	S0/1	-/-



# Example

 

State	Next state/ output	
	input	
	0	1
S0	S1/0	S2/1
S1	S0/1	-
S2	-	S0/0

 

State	Next state/ output	
	input	
	0	1
S0	S1/0	S3/1
S1	S2/1	-
S2	-	S0/1
S3	S1/0	S3/0



# Constraints

- Each vertex describes only one state
- Each edge describes exactly one transaction from current state to the next state
- Each vertex has all out-going edges
- At one edge, there is only one out-going edge at one time



## BCD to Excess-3 code Converter

Decimal digit	BCD	Excess-3
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100

Excess-3 is self-complementing


- $6_{10} = 0110_2$
- $6_{\text{excess-3}} = 0110_2 + 0011_2 = 1001_2$



# Input/output Relation

Bin = 8 (BCD)

Bout = 8 (Excess-3)

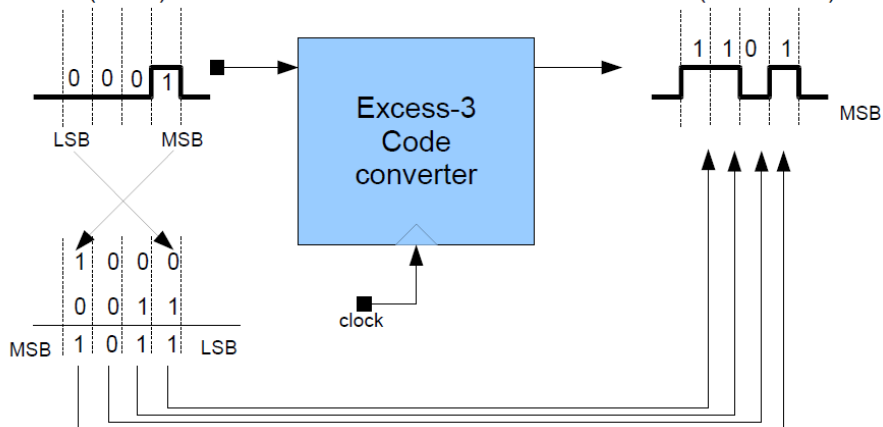


Input-output bit stream in a BCD to Excess-3 serial code converter



# State Transaction Graph – State Transaction Table

State transition graph (Mealy)

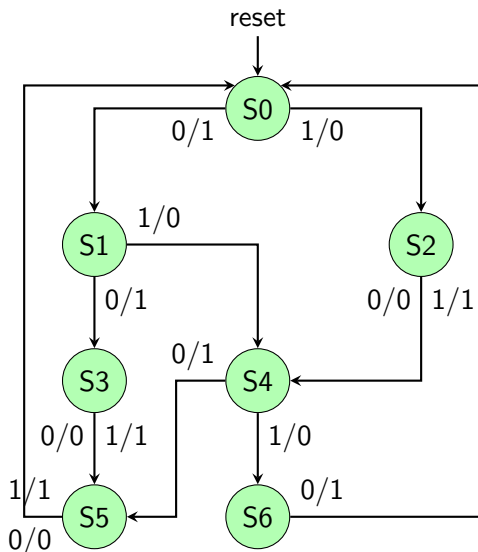

State transition table (Mealy)

State	Next state/ output	
	input	
	0	1
S0	S1/1	S2/0
S1	S3/1	S4/0
S2	S4/0	S4/1
S3	S5/0	S5/1
S4	S5/1	S6/0
S5	S0/0	S0/1
S6	S0/1	-/-



# State Encoding

- States are stored by FFs
- 7 states, using 3 FFs

State assignment	
$q_2 q_1 q_0$	State
000	S0
001	S1
010	S6
011	S4
100	-
101	S2
110	S5
111	S3

State $q_2 q_1 q_0$	Next state $q_2^+ q_1^+ q_0^+$		output	
	Input		Input	
	0	1	0	1
000 (S0)	001	101	1	0
001 (S1)	111	011	1	0
101 (S2)	011	011	0	1
111 (S3)	110	110	0	1
011 (S4)	110	010	1	0
110 (S5)	000	000	0	1
010 (S6)	000	-	1	-
100 (-)	-	-	-	-



# Simplify State Transaction Function

		$q_0 B_{in}$			
		00	01	11	10
$q_2 q_1$	00	1	1	1	1
	01	0	x	0	0
	11	0	0	0	0
	10	x	x	1	1

$q_0^+ = q_1'$

		$q_0 B_{in}$			
		00	01	11	10
$q_2 q_1$	00	0	0	1	1
	01	0	x	1	1
	11	0	0	1	1
	10	x	x	1	1

$q_1^+ = q_0$

		$q_0 B_{in}$			
		00	01	11	10
$q_2 q_1$	00	0	1	0	1
	01	0	x	0	1
	11	0	0	1	1
	10	x	x	0	0

$$q_2' = q_1' q_0' B_{in} + q_2' q_0 B_{in}' + q_2 q_1 q_0$$


		$q_0 B_{in}$			
		00	01	11	10
$q_2 q_1$	00	1	0	0	1
	01	1	x	0	1
	11	0	1	1	0
	10	x	x	1	0

$$B_{out} = q_2' B_{in}' + q_2 B_{in} \equiv$$





# Implementing BCD to Excess-3 Converter

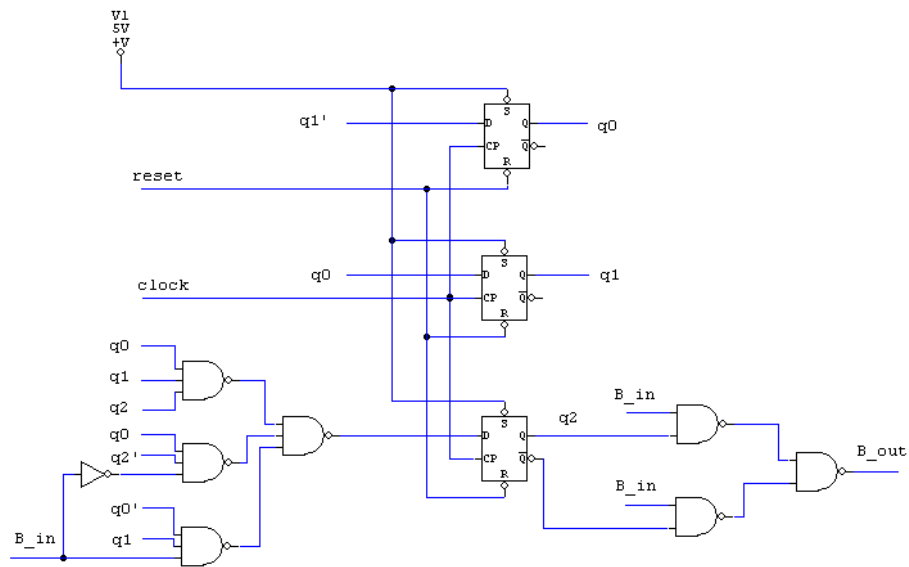


# FSM Example: Serial-Line Code Converter

- 3 signals:
  - Clock
  - Handshaking signal
  - Data
- Well-known encoding algorithms:
  - NRZ
  - NRZI: if input is 1, the previous output value is inversed while 0 input keeps output unchanged
  - RZ: if input is 1, output is 1 during the first half cycle and 0 during the second half cycle while 0 input produces 0 output
  - Manchester: if input is 0, output is 0 during the first half cycle and 1 during the second half cycle while 1 input produces 1 output during the first half and 0 output during the second half



# Serial Encoding Examples

 


Clock\_2's frequency is double clock\_1's frequency to implement the NRZI, RZ, and Manchester encoding algorithms


 
# Mealy FSM for Serial Encoding

- The Manchester algorithm
  - Waiting state (S0)
  - Just receiving 1 state (S2)
  - Just receiving 0 state (S1)



state	$q_1 q_0$
S0	00
S1	01
S2	10

State	Next state/ output	
	input	
	0	1
S0	S1/0	S2/1
S1	S0/1	-
S2	-	S0/0

State $q_1 q_0$	Next state $q_1^+ q_0^+$		output	
	Input		Input	
	0	1	0	1
00 (S0)	01	10	0	1
01 (S1)	00	00	1	-
10 (S2)	00	00	-	0



# Implementing the Mealy FSM

		$B_{in}$	
		0	1
$q_1 q_0$	00	0	1
	01	0	0
11		-	-
10		0	0


$$q_1^+ = q_1' q_0' B_{in}$$

		$B_{in}$	
		0	1
$q_1 q_0$	00	1	0
	01	0	0
11		-	-
10		0	0

$$q_0^+ = q_1' q_0' B_{in}'$$

		$B_{in}$	
		0	1
$q_1 q_0$	00	0	1
	01	1	1
11		-	-
10		0	0


$$B_{out} = q_1' q_0 + q_1' B_{in}$$

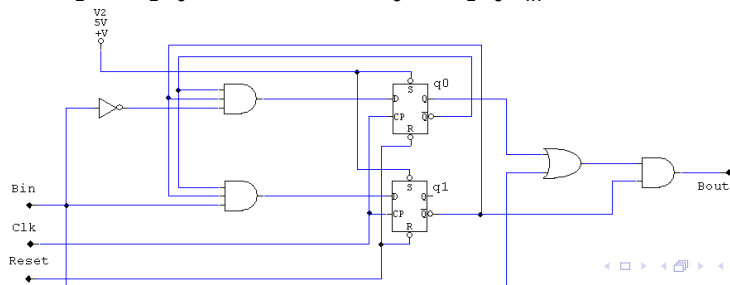

# Moore FSM for Serial Encoding
 
## The Manchester Algorithm

- S0: starting/second half of the cycle receiving 1, the output is 0
- S1: first half of the cycle receiving 0, the output is 0
- S2: second half of the cycle receiving 0, the output is 1
- S3: first half of the cycle receiving 1, the output is 1



State	Next state/ output	
	input	
	0	1
S0	S1/0	S3/1
S1	S2/1	-
S2	-	S0/1
S3	S1/0	S3/0

State $q_1 q_0$	Next state $q_1^+ q_0^+$		output
	Input		
	0	1	
00 (S0)	01	11	0
01 (S1)	10	-	0
11 (S3)	-	00	1
10 (S2)	01	11	1



# Implementing the Moore FSM

	$B_{in}$	
	0	1
$q_1 q_0$		
00	0	1
01	1	x
11	-	0
10	0	1


$$q_1^+ = q_0' B_{in} + q_1' q_0$$

	$B_{in}$	
	0	1
$q_1 q_0$		
00	1	1
01	0	-
11	-	0
10	1	1

$$q_0^+ = q_0'$$

	$B_{in}$	
	0	1
$q_0$		
0	0	0
1	1	1

$$B_{out} = q_0$$

 

## Simplify Equivalent States


- Two states are equivalent:
  - Output and the next states are the same in all inputs (c1)
  - Can be combined together without any changed behavior (c2)
- Reducing two equivalent states reduces hardware cost
- Each FSM has **one and only one simplest equivalent FSM**

State	Next state		output	
	Input	Input	Input	Input
	0	1	0	1
S0	S6	S3	0	0
S1	S1	S6	0	1
S2	S2	S5	0	1
S3	S7	S3	0	1
S4	S7	S2	0	0
S5	S7	S2	0	0
S6	S0	S1	0	0
S7	S4	S3	0	0





## Simplify Equivalent States example


 


State	Next state		output	
	Input 0	Input 1	Input 0	Input 1
S0	S6	S3	0	0
S1	S1	S6	0	1
S2	S2	S5	0	1
S3	S7	S3	0	1
S4	S7	S2	0	0
S5	S7	S2	0	0
S6	S0	S1	0	0
S7	S4	S3	0	0


  
# Simplify Equivalent States Algorithm

- Step 1: Find basic equivalent states (c1)



# Simplify Equivalent States Algorithm

- Step 2: Create a possible equivalent states table (c2)
  - Let impossible equivalent cells be empty
  - Fill conditions upon which two corresponding states can be equivalent

S <sub>1</sub>						
S <sub>2</sub>		S <sub>6</sub> S <sub>4</sub>				
S <sub>3</sub>		S <sub>1</sub> S <sub>7</sub> S <sub>6</sub> S <sub>3</sub>	S <sub>2</sub> S <sub>7</sub> S <sub>4</sub> S <sub>3</sub>			
S <sub>4</sub>	S <sub>6</sub> S <sub>7</sub> S <sub>3</sub> S <sub>2</sub>					
S <sub>6</sub>	S <sub>3</sub> S <sub>1</sub>			S <sub>7</sub> S <sub>0</sub> S <sub>2</sub> S <sub>1</sub>		
S <sub>7</sub>	S <sub>6</sub> S <sub>4</sub>			S <sub>2</sub> S <sub>3</sub>	S <sub>0</sub> S <sub>4</sub> S <sub>1</sub> S <sub>3</sub>	
	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	S <sub>4</sub>	S <sub>6</sub>

S<sub>1</sub> và S<sub>0</sub> không thể tương đương

S<sub>2</sub> và S<sub>1</sub> tương đương khi S<sub>6</sub> và S<sub>4</sub> tương đương

State	Next state		Output	
	0	1	0	1
S <sub>0</sub>	S <sub>6</sub>	S <sub>3</sub>	0	0
S <sub>1</sub>	S <sub>1</sub>	S <sub>6</sub>	0	1
S <sub>2</sub>	S <sub>2</sub>	S <sub>4</sub>	0	1
S <sub>3</sub>	S <sub>7</sub>	S <sub>3</sub>	0	1
S <sub>4</sub>	S <sub>7</sub>	S <sub>2</sub>	0	0
S <sub>6</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
S <sub>7</sub>	S <sub>4</sub>	S <sub>3</sub>	0	0

# Simplify Equivalent States Algorithm

- Step 3: Consider equivalent conditions of any two states, delete corresponding cell if the cell contains any inequivalent couple

